

1. Find the current I in the circuit shown Fig. 1.

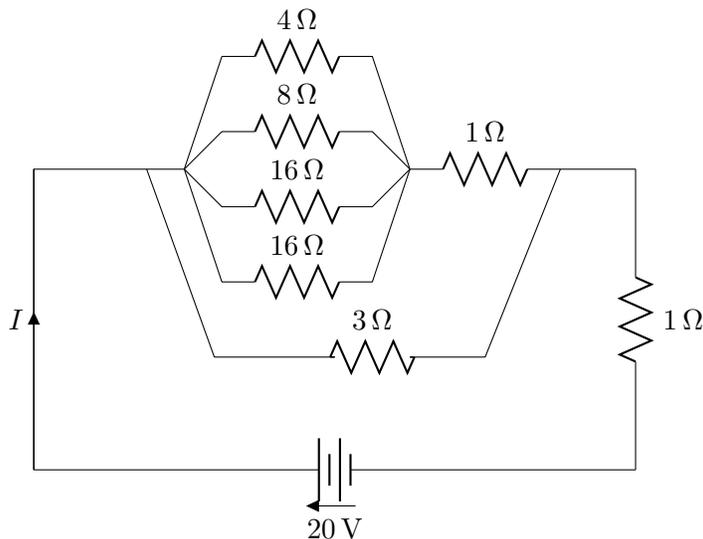


Figure 1: Problem 1.

2. In the circuit shown in Fig. 2, the power produced by bulb₁ and bulb₂ is 1 kW and 50 W, respectively. Which light has the higher resistance? (Assume the resistance of the light bulb remains constant with time.)

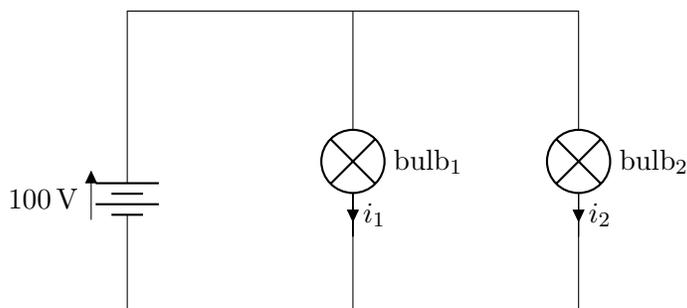


Figure 2: Problem 2.

3. A regular tetrahedron is a pyramid with a triangular base. Six $R = 10.0 \Omega$ resistors are placed along its six edges, with junctions at its four vertices, as shown in Fig. 3. A 12.0-V battery is connected to any two of the vertices. Find (i) the equivalent resistance of the tetrahedron between these vertices and (ii) the current in the battery.
4. Find the equivalent resistance in the limit $n \rightarrow \infty$ for the circuits shown in Figs. 4 and 5.

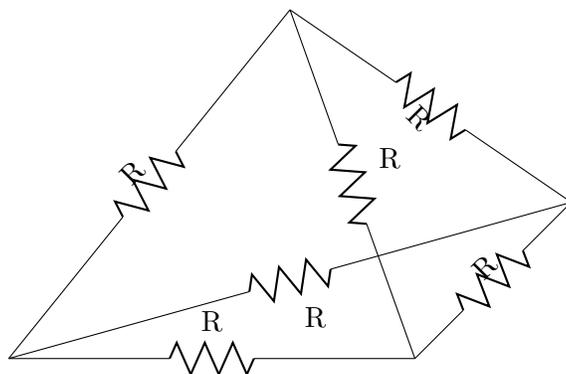


Figure 3: Problem 3.

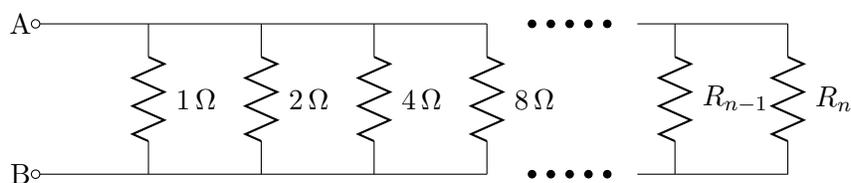


Figure 4: Problem 4 (i).

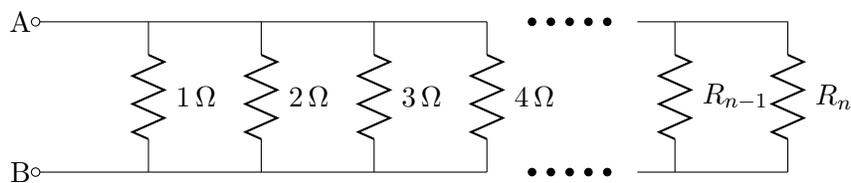


Figure 5: Problem 4 (ii).

5. Determine the magnitude and directions of the currents through $R_1 = 22 \Omega$ and $R_2 = 15 \Omega$ in the circuit of Fig. 6. The batteries have an internal resistance of $r = 1.2 \Omega$.

6. Determine the magnitude and directions of the currents in each resistor shown in Fig. 7. The batteries has emfs of $\varepsilon_1 = 9 \text{ V}$ and $\varepsilon_2 = 12 \text{ V}$ and the resistors have values of $R_1 = 25 \Omega$, $R_2 = 18 \Omega$, and $R_3 = 35 \Omega$.

7. For the circuit shown in Fig. 8, calculate (i) the current in the 2.00Ω resistor and (ii) the potential difference between points a and b .

8. Consider the circuit shown in Fig. 9, with the start up switch T_1 open (for a long time). Now, close the switch and wait for a while. What is the change in the total charge of the capacitor?

9. The circuit in Fig. 10 has been connected for a long time. (i) What is the voltage across the capacitor? (ii) If the battery is disconnected, how long does it take the capacitor to discharge to one tenth of its initial voltage?

10. Find the voltage across A and B (i.e. V_{AB}) as a function of time in the circuit shown in

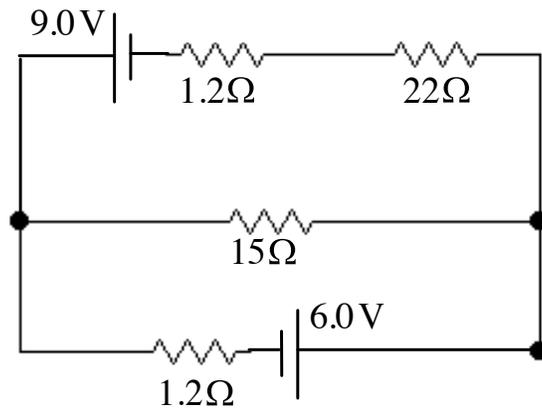


Figure 6: Problem 5.

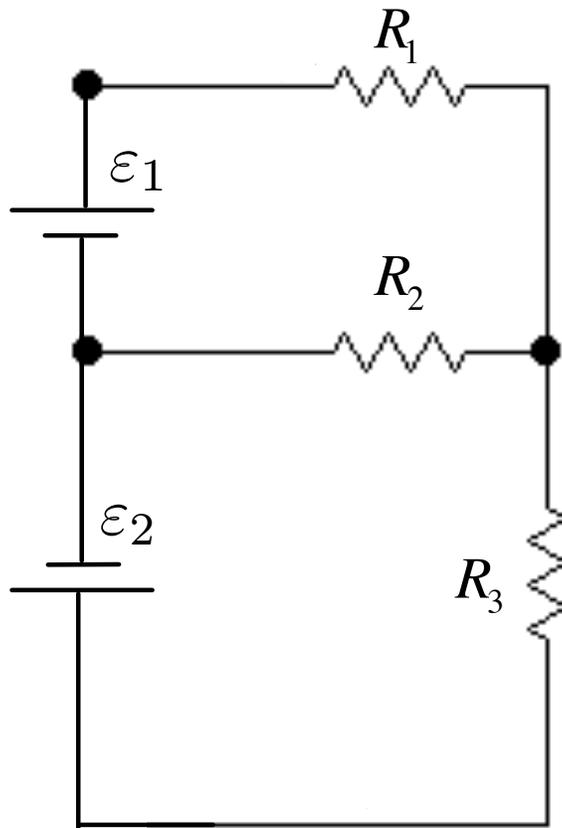


Figure 7: Problem 6.

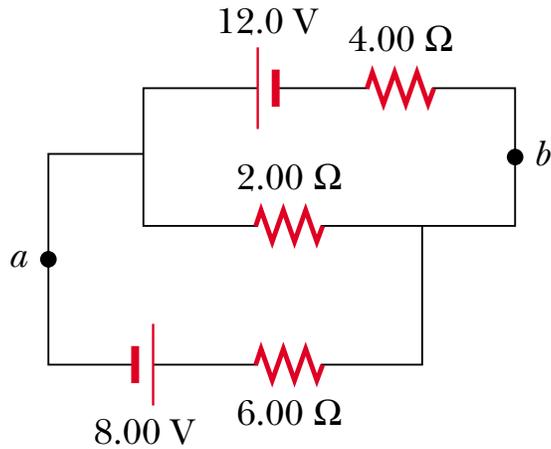


Figure 8: Problem 7.

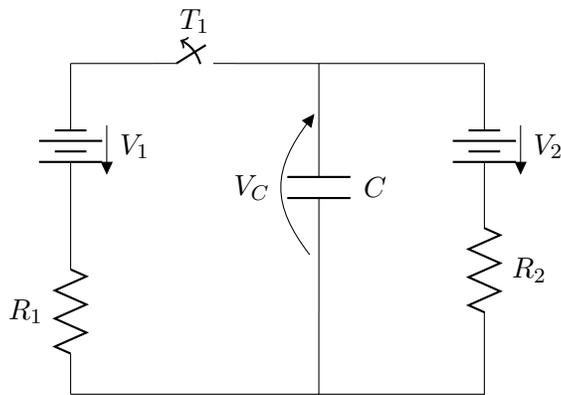


Figure 9: Problem 8.

Fig. 11.

Enrichment Problems

11. The switch in Fig. 12(a) closes when $\Delta V_c > 2\Delta V/3$ and opens when $\Delta V_c < \Delta V/3$. The voltmeter reads a voltage as plotted in Fig. 12(b). What is the period T of the waveform in terms of R_1 , R_2 , and C ?

12. This problem illustrates how a digital voltmeter affects the voltage across a capacitor in an RC circuit. A digital voltmeter of internal resistance r is used to measure the voltage across a capacitor after the switch in Fig. 13 is closed. Because the meter has finite resistance, part of the current supplied by the battery passes through the meter. (i) Apply Kirchhoff's rules to this

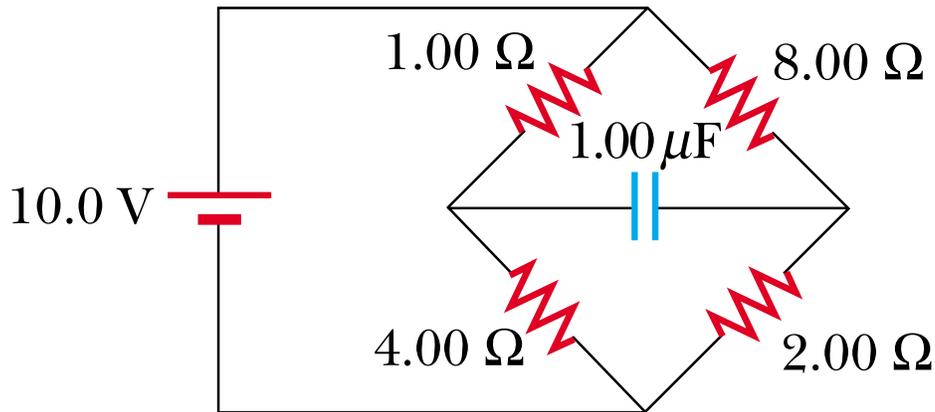


Figure 10: Problem 9.

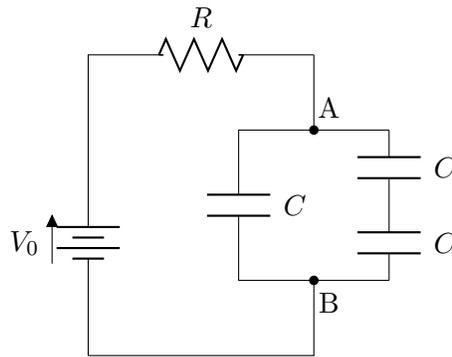


Figure 11: Problem 10.

circuit, and use the fact that $i_C = dq/dt$ to show that this leads to the differential equation

$$R_{\text{eq}} \frac{dq}{dt} + \frac{q}{C} = \frac{r}{r+R} \mathcal{E},$$

where $R_{\text{eq}} = rR/(r+R)$. (ii) Show that the solution to this differential equation is


$$q = \frac{r}{r+R} C \mathcal{E} \left(1 - e^{-t/(R_{\text{eq}}C)} \right)$$

and that the voltage across the capacitor as a function of time is


$$V_C = \frac{r}{r+R} \mathcal{E} (1 - e^{-t/(R_{\text{eq}}C)}).$$

(iii) If the capacitor is fully charged, and the switch is then opened, how does the voltage across the capacitor behave in this case?

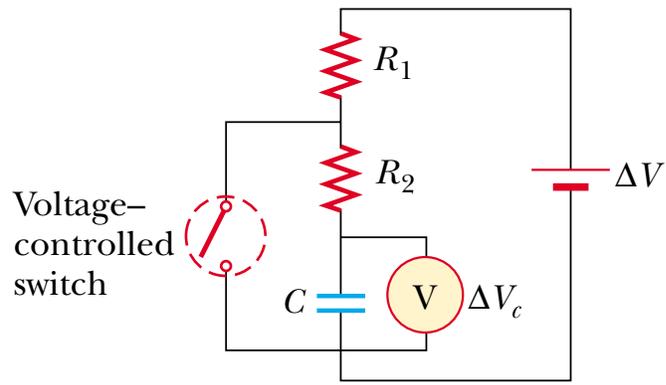13. When two slabs of n -type and p -type semiconductors are put in contact, the relative affinities of the materials cause electrons to migrate out of the n -type material across the junction to the p -type material. This leaves behind a volume in the n -type material that is positively charged and



(a)

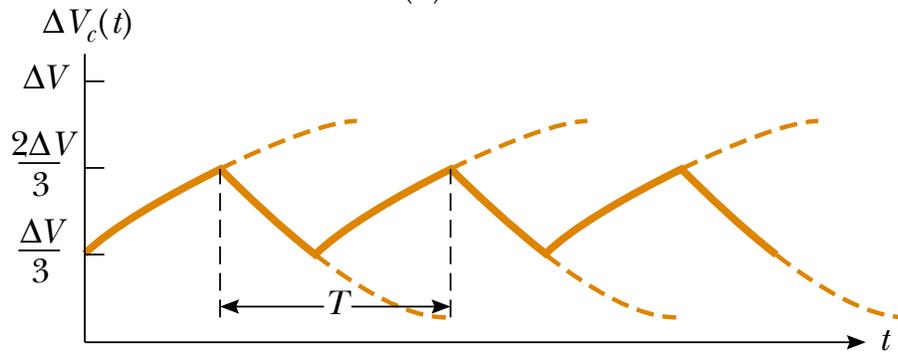

(b)

Figure 12: Problem 11.

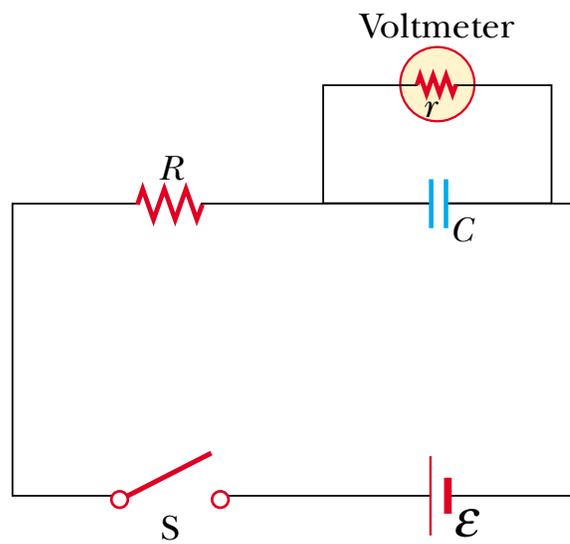


Figure 13: Problem 12.

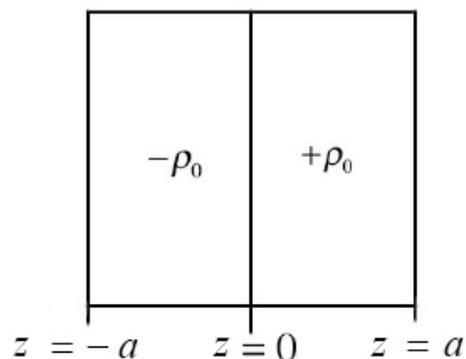


Figure 14: Problem 13.

creates a negatively charged volume in the p -type material. Let us model this as two infinite slabs of charge, both of thickness a with the junction lying on the plane $z = 0$. The n -type material lies in the range $0 < z < a$ and has uniform charge density $+\rho_0$. The adjacent p -type material lies in the range $-a < z < 0$ and has uniform charge density $-\rho_0$; see Fig. 14. Hence:

$$\rho(x, y, z) = \rho(z) = \begin{cases} +\rho_0 & 0 < z < a \\ -\rho_0 & -a < z < 0 \\ 0 & |z| > a \end{cases} .$$

(i) Find the electric field everywhere. (ii) Find the potential difference between the points P_1 and P_2 . The point P_1 is located on a plane parallel to the slab a distance $z_1 > a$ from the center of the slab. The point P_2 is located on plane parallel to the slab a distance $z_2 < -a$ from the center of the slab.